
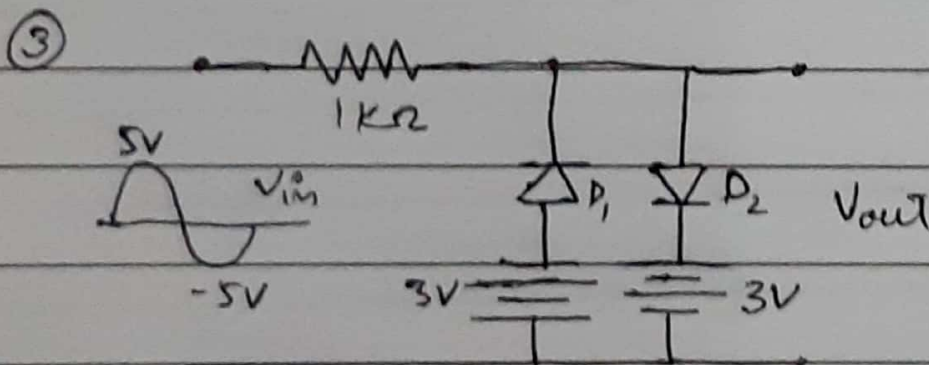
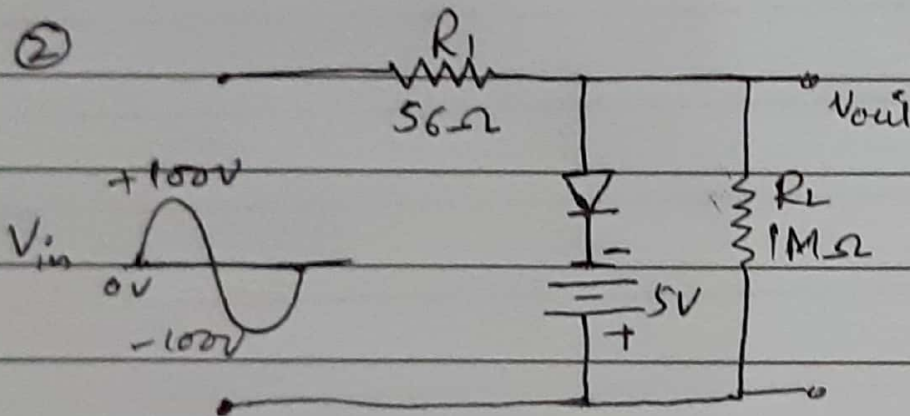


# Assignment

Date: 28-10-2020

Determine The output voltage waveform.

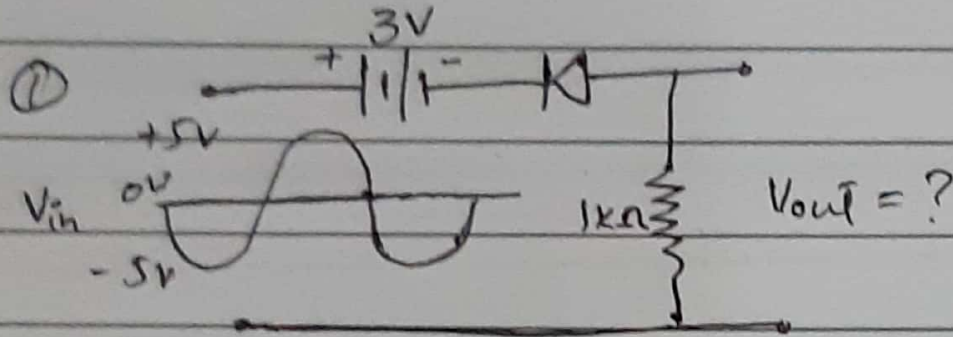

④ Explain the positive limiter and negative clamper.